



Fundamental Algorithms for System Modeling, Analysis, and Optimization

Edward A. Lee, Jaideep
Roychowdhury, Sanjit A. Seshia

UC Berkeley
EECS 144/244

Copyright © 2010-date, E. A. Lee, J. Roychowdhury,
S. A. Seshia, All rights reserved

Boolean Algebra and Logic Optimization- 2

Thanks to S. Devadas, K. Keutzer, S. Malik, R. Rutenbar for several slides

Multi-level Logic Optimization: Outline

Overview of Multi-level Optimization: An Example


Core Concepts:

- Boolean Function Decomposition

- Boolean and Algebraic Division

- Identifying Divisors

Representation: Boolean Network

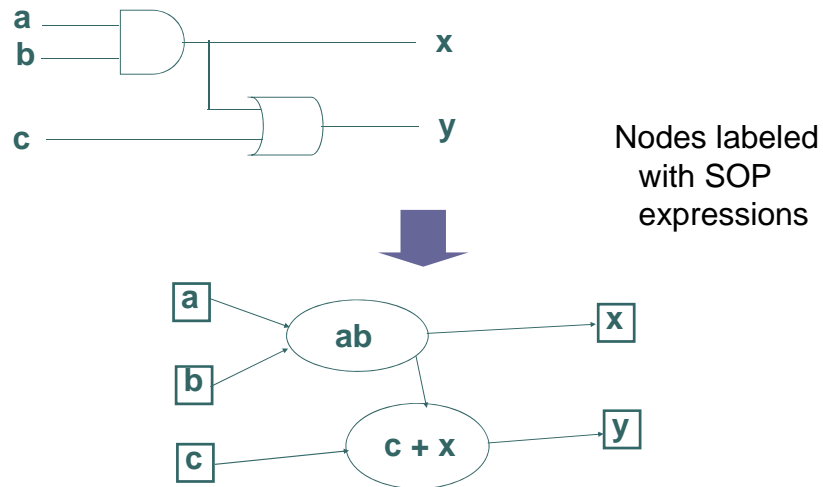

EECS 144/244, UC Berkeley: 3

Boolean Network, Explained

It's a graph:

- ❑ Primary inputs (variables)
- ❑ Primary outputs
- ❑ Intermediate nodes (in SOP form in terms of its inputs)

- ❑ Quality of network: area, delay, ...
 - measured in terms of $\#(\text{literals})$, depth, ...

EECS 144/244, UC Berkeley: 4

Tech.-Independent Multi-Level Optimization: Operations on Boolean Network

Involves performing the following operations “iteratively” until “good enough” result is obtained:

1. **Simplification**

Minimizing two-level logic function (SOP for a single node)

2. **Elimination**

Substituting one expression into another.

3. **Decomposition**

Expressing a single SOP with 2 or more simpler forms

4. **Extraction**

Finding & pulling out subexpressions common to many nodes


5. **Substitution**

Like extraction, but nodes in the network are re-used

EECS 144/244, UC Berkeley: 5

Example


(due to G. De Micheli)

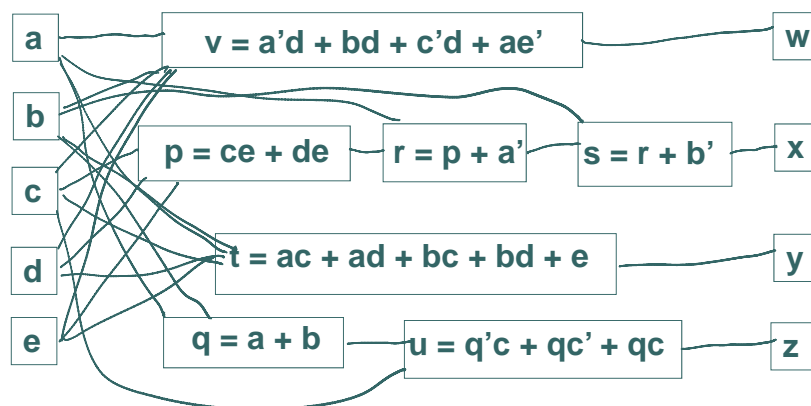

#literals = 33, depth = 3

EECS 144/244, UC Berkeley: 6


Example: Elimination

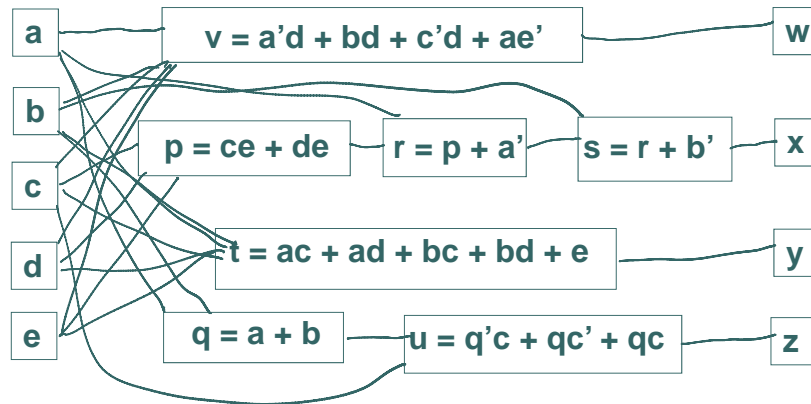

#literals = 33, depth = 3

EECS 144/244, UC Berkeley: 7


Example: Eliminate node r

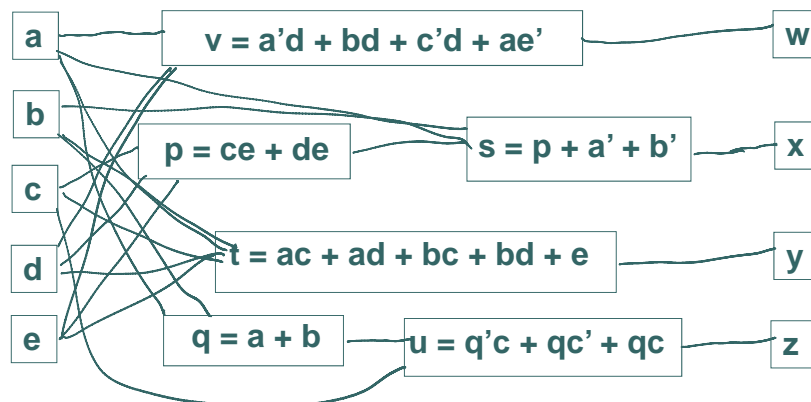

#literals = 32, depth = 2

EECS 144/244, UC Berkeley: 8


Example: Simplification

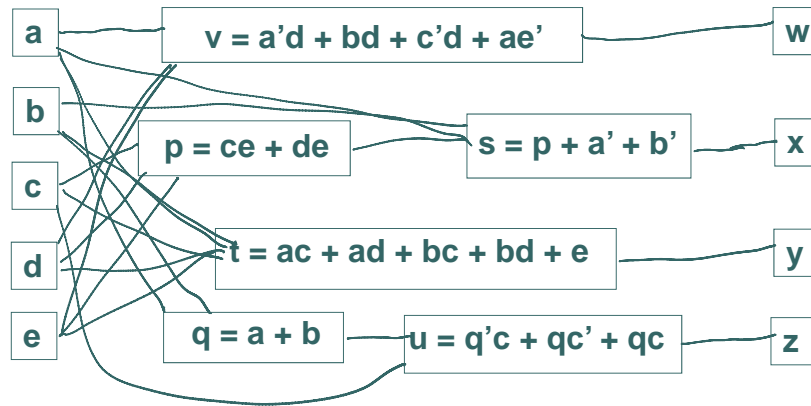

#literals = 32, depth = 2

EECS 144/244, UC Berkeley: 9


Example: Simplifying node u

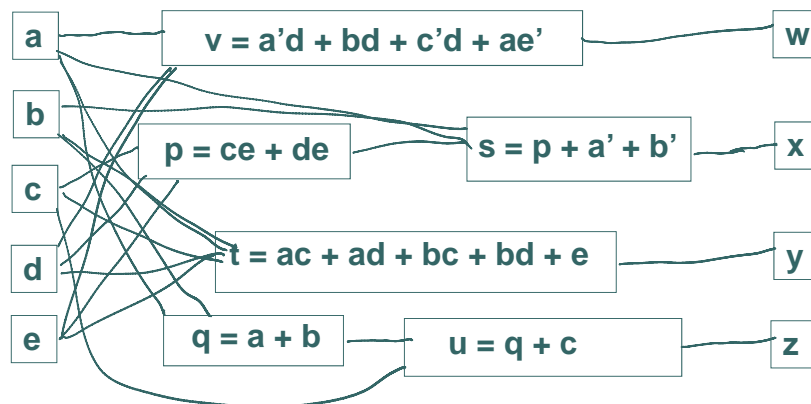

#literals = 28, depth = 2

EECS 144/244, UC Berkeley: 10


Example: Decomposition

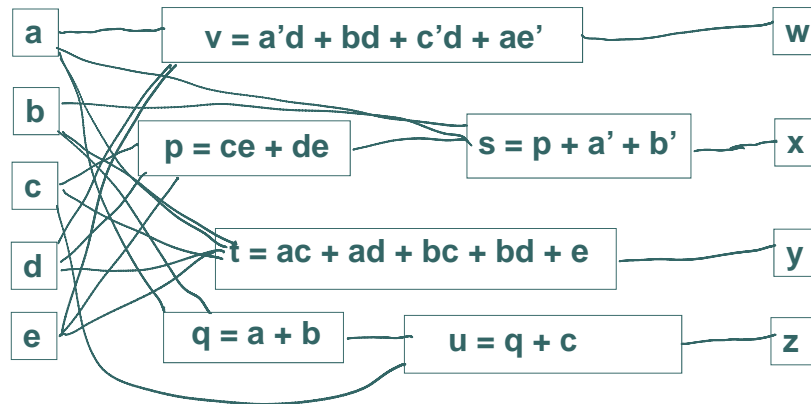

#literals = 28, depth = 2

EECS 144/244, UC Berkeley: 11


Example: Decomposing node v

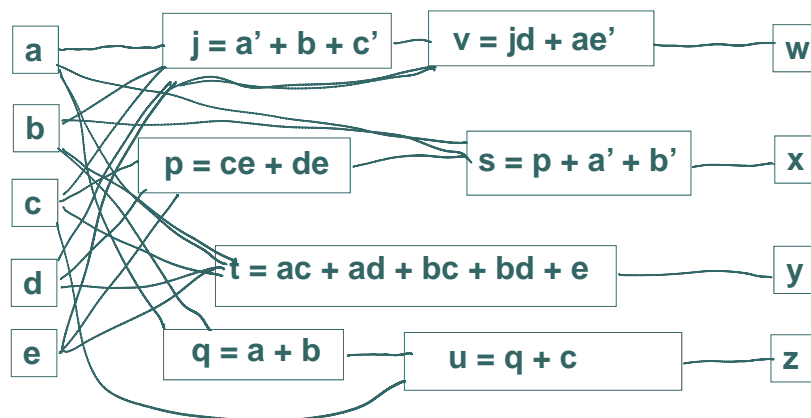

#literals = 27, depth = 2

EECS 144/244, UC Berkeley: 12


Example: Extraction

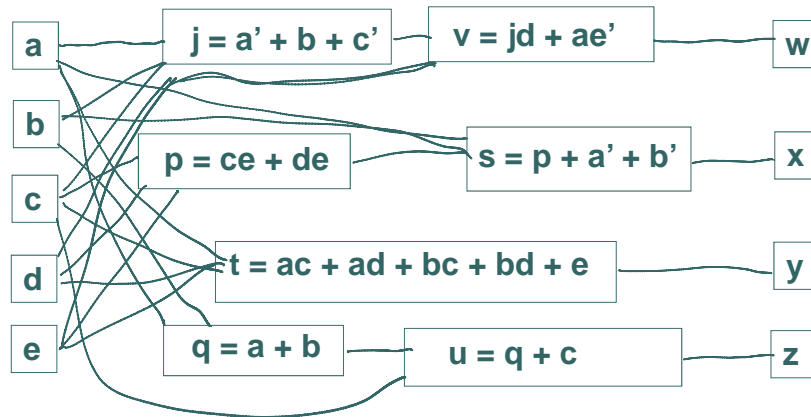

#literals = 27, depth = 2

EECS 144/244, UC Berkeley: 13


Example: Extracting from p and t

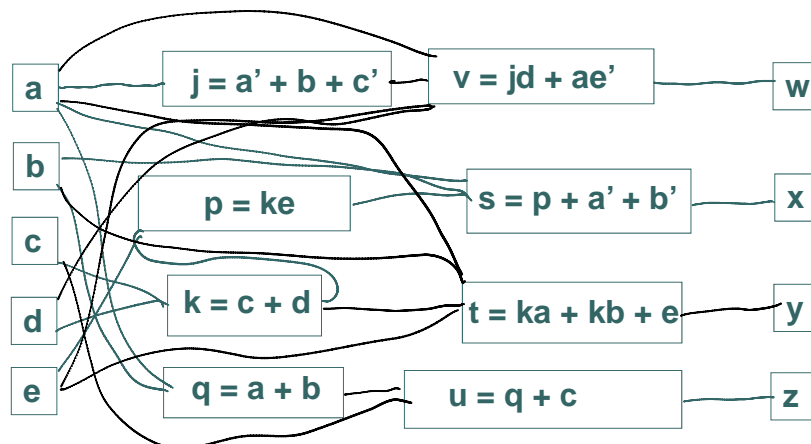

#literals = 23, depth = 3

EECS 144/244, UC Berkeley: 14

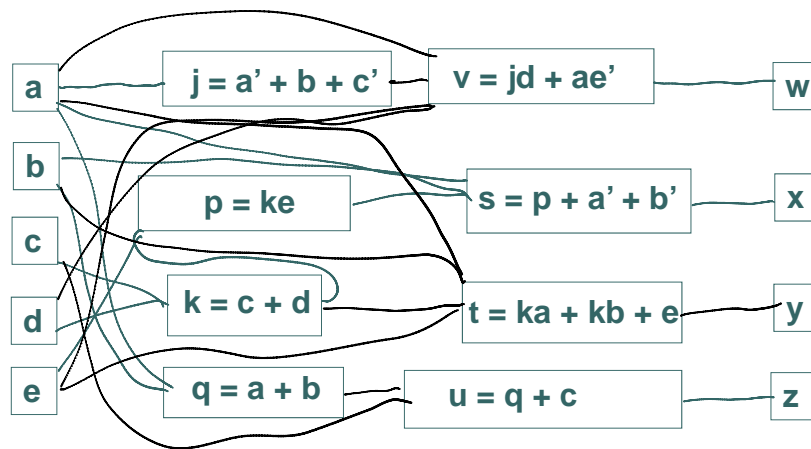Example: What next? Can we improve further?



#literals = 23, depth = 3

EECS 144/244, UC Berkeley: 15

Which Operations Do We Know How to Do?

1. **Simplification**
Minimizing two-level logic function (SOP for a single node)
2. **Elimination**
Substituting one expression into another.
3. **Decomposition**
Expressing a single SOP with 2 or more simpler forms
4. **Extraction**
Finding & pulling out subexpressions common to many nodes
5. **Substitution**
Like extraction, but nodes in the network are re-used

EECS 144/244, UC Berkeley: 16

Decomposition by Factoring/Division

Starting with a SOP Form

$$f = ac + ad + bc + bd + ae'$$

We want to generate an equivalent Factored form

$$f = (a + b)(c + d) + ae'$$

Reason: Factored forms are 'natural' multi-level representations – tree-like expressions

To do factoring, we need to

- ❑ Identify divisors
- ❑ Perform division

EECS 144/244, UC Berkeley: 17

Divisors and Decomposition

Given Boolean function F , we want to write it as

$$F = D \cdot Q + R$$

where D – Divisor, Q – Quotient, R – Remainder

Decomposition: Searching for divisors which are common to many functions in the network

- identify divisors which are common to several functions
- introduce common divisor as a new node
- re-express existing nodes using the new divisor

EECS 144/244, UC Berkeley: 18

Topics

What is division?

- Boolean vs. Algebraic

How to perform division

How to identify divisors

EECS 144/244, UC Berkeley: 19

Boolean Division

Given Boolean function F , we want to write it as

$$F = D \cdot Q + R$$

Definition:


D is a **Boolean divisor** of F if Q and R exist such that $F = DQ + R$, $DQ \neq 0$. ($F \neq 0$)

D is said to be a **factor** of F if, D is a divisor of F and in addition, $R = 0$; i.e., $F = DQ$.

EECS 144/244, UC Berkeley: 20

Boolean Division: Key Results

 - D is a factor of F iff $F \cdot D' = 0$
 - ON-SET(D) contains ON-SET(F)
- $F \cdot D \neq 0$ iff D is a divisor of F
- How many possible factors D can there be for a given F ?



EECS 144/244, UC Berkeley: 22

Boolean Division: Proof Ideas

D is a factor of F iff $F \cdot D' = 0$

- (only if part): $F = DQ$, so $F \cdot D' = 0$
- (if part): Given that $F \cdot D' = 0$, $F \subseteq D$, so $F = DF$, or $F = D(F+X)$ where $X \cdot D = 0$.
Thus, $F = DH$ for some H .

$F \cdot D \neq 0$ iff D is a divisor of F

- (if): $F = DQ + R$, $FD = DQ + DR$, since $DQ \neq 0$, $FD \neq 0$
- (only if): $FD \neq 0$ and $F = FD + FD'$, take $Q=F+d$, $R=FD'$, where $dD = 0$.

How many possible factors D can there be for a given F ?

- Doubly exponential in number of variables

EECS 144/244, UC Berkeley: 23

Algebraic Model

Idea: Perform division using only the rules (axioms) of real numbers, not all of Boolean algebra

Real Numbers

$a.b = b.a$
 $a+b = b+a$
 $a.(b.c) = (a.b).c$
 $a+(b+c) = (a+b)+c$
 $a.(b+c) = a.b + a.c$
 $a.1 = a \quad a.0 = 0 \quad a+0 = a$

Boolean Algebra

$a.b = b.a$
 $a+b = b+a$
 $a.(b.c) = (a.b).c$
 $a+(b+c) = (a+b)+c$
 $a.(b+c) = a.b + a.c$
 $a.1 = a \quad a.0 = 0 \quad a+0 = a$

$a+(b.c) = (a+b).(a+c)$
 $a+a' = 1 \quad a.a' = 0 \quad a.a = a$
 $a+a = a$
 $a+1 = 1 \quad a+ab = a \quad a.(a+b) = a$
 \dots

EECS 144/244, UC Berkeley: 24

Algebraic Division

- ❑ A literal and its complement are treated as unrelated

Each literal as a fresh variable

E.g.

$$f = ab + a'x + b'y \quad \text{as} \quad f = ab + dx + ey$$

- ❑ Treat SOP expression as a polynomial

Division/factoring then becomes polynomial division/factoring

- ❑ Boolean identities are ignored

- Except in pre-processing
- Simple local simplifications like $a + ab \rightarrow a$ performed

EECS 144/244, UC Berkeley: 25

Algebraic vs. Boolean factorization

$$f = a\bar{b} + a\bar{c} + b\bar{a} + b\bar{c} + c\bar{a} + c\bar{b}$$

Algebraic factorization produces

$$f = a(\bar{b} + \bar{c}) + \bar{a}(b + c) + b\bar{c} + c\bar{b}$$

Boolean factorization produces

$$f = (a + b + c)(\bar{a} + \bar{b} + \bar{c})$$

EECS 144/244, UC Berkeley: 26

Algebraic Division Example

$$F = ac + ad + bc + bd + ae$$

Find Q, R, where $F = DQ + R$ for

1. $D = a + b$

2. $D = a$

EECS 144/244, UC Berkeley: 27

Algebraic Division Algorithm

What we want: $|F| \mid |D|$

Given F, D , find Q, R

F, D expressed as sets of cubes (same for Q, R)

Approach:

For each cube C in D { $|F|$

let $B = \{\text{cubes in } F \text{ contained in } C\}$

• if (B is empty) return $Q = \{ \}$, $R = F$

let $B = \{\text{cubes in } B \text{ with variables in } C \text{ removed}\}$

if (C is the first cube in D we're looking at)

let $Q = B$;

else $Q = Q \cap B$;

}

$R = F \setminus (Q \times D)$;

$|D|$

$|F|$

$|F|$

Complexity?

EECS 144/244, UC Berkeley: 28

Taking Stock

□ What we know:

- How to perform Algebraic division given a divisor D

□ What we don't

- How to find a divisor D ?

□ Recall what we wanted to do:

Given 2 functions F and G , find a common divisor D and factorize them as

$$F = D Q_1 + R_1$$

$$G = D Q_2 + R_2$$

EECS 144/244, UC Berkeley: 29

New Terminology: Kernels

A kernel of a Boolean expression F is a **cube-free expression** that results when you divide F by a single cube

- That “single cube” is called a co-kernel

Cube-free expression: Cannot factor out a single cube that leaves behind no remainder

Examples: Which are cube-free?

- $F1 = a + b$ ✓
- $F2 = \underline{abc} + \underline{abd}$ ✗

EECS 144/244, UC Berkeley: 30

Kernels: Examples

$$F = ae + be + cde + ab$$

$K(f)$

Kernel	Co-kernel
$\{a,b,cd\}$	e
$\{e,b\}$	$?$
$?$	b
$\{ae,be,cde,ab\}$	$?$

Note: can view kernels as sets of cubes

EECS 144/244, UC Berkeley: 31

Why are Kernels Useful?

Multi-level logic optimizer wants to find common divisors of two (or more) functions f and g

Theorem: [Brayton & McMullen]

f and g have a non-trivial (multiple-cube) common divisor d if and only if there exist kernels $k_f \in K(f)$, $k_g \in K(g)$ such that $k_f \cap k_g$ is non-trivial, i.e., not a cube

(here set intersection is applied to the sets of cubes in k_f and k_g)

\therefore can use kernels of f and g to locate common divisors

EECS 144/244, UC Berkeley: 32

Theorem, Sketched Informally

$$F = D1 \cdot K1 + R1$$

$$G = D2 \cdot K2 + R2$$

$$K1 = (X + Y + \dots) + \text{stuff1}$$

$$K2 = (X + Y + \dots) + \text{stuff2}$$

Then,

- $F = (X + Y + \dots) D1 + \text{stuff3}$

- $G = (X + Y + \dots) D2 + \text{stuff4}$

So, if we find kernels and intersect them, the intersection gives us our common divisor

EECS 144/244, UC Berkeley: 33

Kernel Intersection: Example

$$F = ae + be + cde + ab$$

$$G = ad + ae + bd + be + bc$$

$K(f)$

Kernel	Co-kernel
$\{a,b,cd\}$	e
$\{e,b\}$	a
$\{e,a\}$	b
$\{ae,be,cde,ab\}$	1

$K(g)$

Kernel	Co-kernel
$\{a,b\}$	d or e
$\{d,e\}$	a or b
$\{d,e,c\}$	b
$\{ad,ae,bd,be,bc\}$	1

EECS 144/244, UC Berkeley: 34


How do we find Kernels?

Overview: Given a function F

1. Pick a variable x appearing in F , and use it as a divisor
2. Find the corresponding kernel K if one exists (at least 2 cubes in F contain x)
 - If not, go back to (1) and pick another variable
3. Use K in place of F and recurse to find kernels of K
 - $F = xK + R$ and $K = yM + S \rightarrow F = xyM + \dots$
 - Add kernels of K to those of F
4. Go back to (1) and pick another variable to keep finding kernels


EECS 144/244, UC Berkeley: 35

Finding Kernels: Example

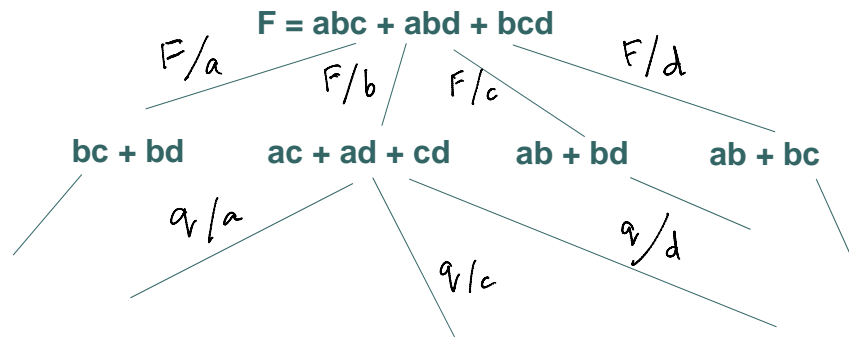

EECS 144/244, UC Berkeley: 36

Finding Kernels: Example

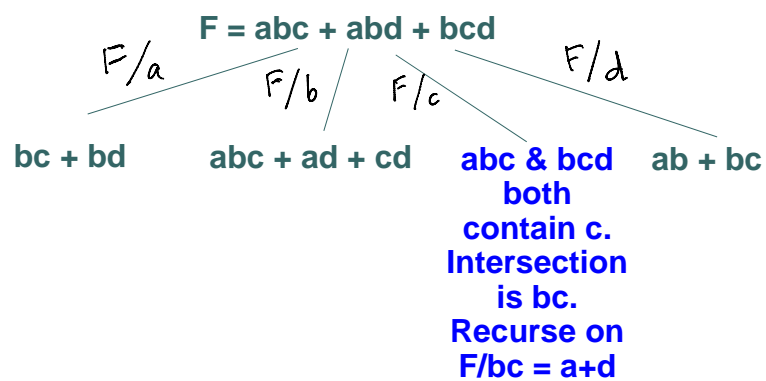

Take intersection of all cubes containing a variable

EECS 144/244, UC Berkeley: 37

Kernel Finding Algorithm

```
FindKernels(F) {  
  K = { };  
  for (each variable x in F) {  
    if (F has at least 2 cubes containing x) {  
      let S = {cubes in F containing x};  
      let c = cube resulting from intersection of all cubes in S  
      K = K  $\cup$  FindKernels(F/c); //recursion  
    }  
  }  
  K = K  $\cup$  F ;  
  return K;  
}
```

EECS 144/244, UC Berkeley: 38

Reading

R. Brayton, G. Hachtel, A. Sangiovanni-Vincentelli,
'Multilevel Logic Synthesis', Proceedings of the IEEE,
Feb'90.

EECS 144/244, UC Berkeley: 40