

# Fundamental Algorithms for System Modeling, Analysis, and Optimization

Edward A. Lee, Jaideep Roychowdhury,  
Sanjit A. Seshia, Stavros Tripakis


UC Berkeley  
EECS 144/244  
Spring 2013

Copyright © 2010-13, E. A. Lee, J. Roychowdhury,  
S. A. Seshia, S. Tripakis. All rights reserved

**Lecture: Timing Analysis, Retiming**

Thanks to Kurt Keutzer for several slides

## RTL Synthesis Flow

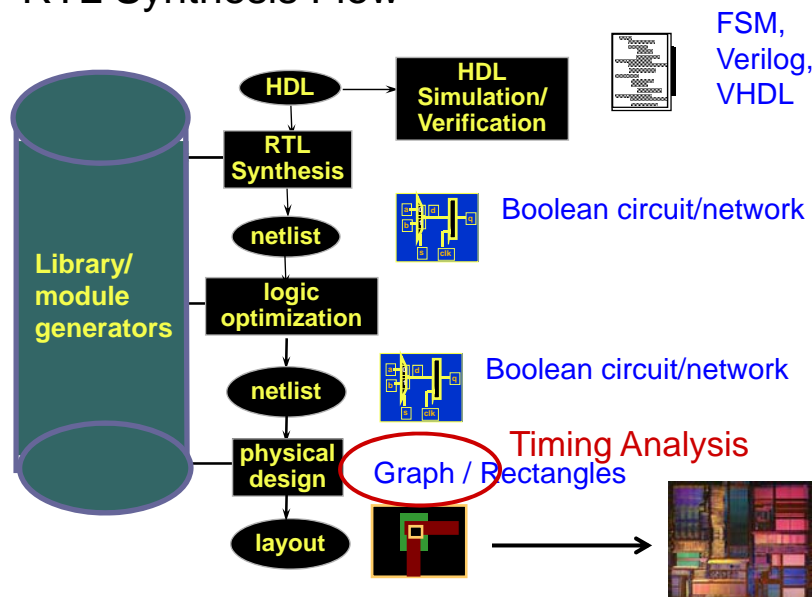

K. Keutzer

EECS 144/244, UC Berkeley: 2

## Timing Analysis / Verification

Verifying a property about **system timing**

Arises in many settings:

- Integrated circuits
- Embedded software
- Distributed embedded systems
- Biological systems
- ...

Here we focus on circuits.

Chapter 15 of Lee-Seshia book contains a more broad discussion.

EECS 144/244, UC Berkeley: 3

## Timing Analysis for Digital ICs


(Clock) Speed is one of the major performance metrics for digital circuits

Timing Analysis = the process of verifying that a chip meets its speed requirement

- E.g., 1 GHz means that next-state function must be computed within 1 ns

EECS 144/244, UC Berkeley: 4

## Static Timing Analysis for Circuits

 

Determine fastest permissible clock speed (e.g. 1 GHz) by determining delay of longest path from register to register (e.g. 1ns.)


EECS 144/244, UC Berkeley: 5

## Cycle Time - Critical Path Delay


Cycle time ( $T$ ) cannot be smaller than longest path delay ( $T_{\max}$ )

Longest (critical) path delay is a function of:

Total gate, wire delays

 

$$T_{\max} \leq T$$

 


EECS 144/244, UC Berkeley: 6

 
## Cycle Time - Setup Time

For FFs to correctly latch data, input data must be stable during:

Setup time ( $T_{\text{setup}}$ ) *before* clock arrives


 
$$T_{\text{max}} + T_{\text{setup}} \leq T$$




EECS 144/244, UC Berkeley: 7

 
## Cycle Time - Clock-skew

If clock network has unbalanced delay – clock skew

Cycle time is also a function of clock skew ( $T_{\text{skew}}$ )


 
$$T_{\text{max}} + T_{\text{setup}} + T_{\text{skew}} \leq T$$




EECS 144/244, UC Berkeley: 8

 
## Cycle Time - Clock to Q

Cycle time is also a function of propagation delay of FF ( $T_{clk-to-Q}$ )

$T_{clk-to-Q}$  : time from arrival of clock signal till change at FF output)



 
$$T_{max} + T_{setup} + T_{skew} + T_{clk-to-Q} \leq T$$



EECS 144/244, UC Berkeley: 9

 
## Min Path Delay - Hold Time

For FFs to correctly latch data, input data must be stable during Hold time ( $T_{hold}$ ) after clock arrives



Determined by delay of shortest path in circuit ( $T_{min}$ ) and clock skew ( $T_{skew}$ )

$$T_{min} \geq T_{hold} + T_{skew}$$

 

EECS 144/244, UC Berkeley: 10

## Summary

Need to be able to compute

$T_{\min}$ : delay of “fastest” path in the circuit

$T_{\max}$ : delay of “slowest” (critical) path in the circuit


EECS 144/244, UC Berkeley: 11

## Modeling Timing in a Combinational Circuit

Arrival time  
in green

Interconnect  
delay in  
red

Gate delay in  
blue

 

What's the right mathematical  
object to use to represent this  
physical object?

EECS 144/244, UC Berkeley: 13

## Modeling - 1

Use a labeled  
*directed graph*


$G = \langle V, E \rangle$

Vertices represent  
gates, primary  
inputs and  
primary outputs

Edges represent  
wires

Labels represent  
delays

What about arrival  
times?

 


EECS 144/244, UC Berkeley: 14

## Modeling - 2

Find longest/shortest  
paths in a *directed*  
graph  $G = \langle V, E \rangle$


What sort of *directed*  
graph do we have?

 Is this in the standard  
form for a  
longest/shortest  
path problem?




EECS 144/244, UC Berkeley: 15

## Split Nodes into Edges

 

EECS 144/244, UC Berkeley: 16

## DAG with Weighted Edges

 


Problem: Find the longest (critical) path from source  $s$  to sink  $f$ .

EECS 144/244, UC Berkeley: 17


 
## Naïve Approach: Enumerate Paths

How many paths in this example?  
In the worst case?



Problem:

Find the longest path from source s to sink f.

EECS 144/244, UC Berkeley: 18

## Algorithm 1: Longest path in a DAG

### Critical Path Method [Kirkpatrick 1966, IBM JRD]

(dynamic programming)

Let  $w(u,v)$  denote weight of edge from  $u$  to  $v$

Steps:

1. Topologically sort vertices (graph is acyclic)

order:  $v_1, v_2, \dots, v_n$      $v_1 = s, v_n = ?$

2. For each vertex  $v$ , compute

$d(v)$  = length of longest path from source  $s$  to  $v$

$d(v_1) = 0$

For  $i = 2..n$

$d(v_i) = \max_{\text{all incoming edges } (u, v_i)} d(u) + w(u, v_i)$

EECS 144/244, UC Berkeley: 19

## Algorithm 1: Longest path in a DAG

Critical Path Method [Kirkpatrick 1966, IBM JRD]

Let  $w(u,v)$  denote weight of edge from  $u$  to  $v$

Steps:

1. Topologically sort vertices Time Complexity?  
order:  $v_1, v_2, \dots, v_n$      $v_1 = s, v_n = f$   $O(m+n)$
2. For each vertex  $v$ , compute  
 $d(v)$  = length of longest path from source  $s$  to  $v$   
 $d(v_1) = 0$   
For  $i = 2..n$   
 $d(v_i) = \max_{\text{all incoming edges } (u, v_i)} d(u) + w(u, v_i)$

Run the CPM on our example

EECS 144/244, UC Berkeley: 20

## Graph vs. Circuit

Delay of a combinational circuit depends on

- Circuit topology (graph model)
- Delay model (e.g., fixed vs. variable)
- Boolean behavior of gates

We have only considered circuit topology so far.


Longest/shortest path found on the graph can be very pessimistic:

- Paths can be FALSE
- Delay values are BOUNDS

EECS 144/244, UC Berkeley: 21
 
## False Paths (consider Transition Mode)

A path is false if it cannot be responsible for the delay of a circuit




Graph model implies path of length 6

y: 22
 
## False Paths

A path is false if it cannot be responsible for the delay of a circuit



Length of  
sensitized path = 5

Graph model implies path of length 6

y: 23


## False vs. True Paths

TRUE path = one that can be responsible for the delay of a circuit

Need techniques to find whether a path is TRUE or FALSE

EECS 144/244, UC Berkeley: 24

 
The Fixed Delay Model: Constant delay for each gate (or wire)




Transition delay is 0, for both input transitions.

EECS 144/244, UC Berkeley: 25
 
## Paradoxical Behavior with the Transition Model?



 Transition delay is 0, for both input transitions.  
Consider the “faster” circuit



non-monotonic  
w.r.t. time delays!

EECS 144/244, UC Berkeley: 26

## Problems with Fixed Delay + Transition Model

1. Transition model can be tricky to reason about
2. Fixed gate delays are unrealistic, due to manufacturing process variations


More realistic delay model: *Lower and upper bounds*

Perform timing analysis for a whole family of circuits that share the same lower/upper bounds

EECS 144/244, UC Berkeley: 27
 
## Fixed Delays $\rightarrow$ Bounded Delays

Want algorithms that report the **critical path delay** of the **slowest circuit** in the circuit family




Paper: *Computation of Floating Mode Delay in Combinational Circuits: Theory and Algorithms*, Devadas, Keutzer, Malik, 1993  
(on bspace)

EECS 144/244, UC Berkeley: 28

## RETIMING

EECS 144/244, UC Berkeley: 29


## Retiming Tradeoffs

 

[Shenoy, 1997]

EECS 144/244, UC Berkeley: 30


## Retiming Tradeoffs

 

[Shenoy, 1997]

EECS 144/244, UC Berkeley: 31


## Retiming Tradeoffs

 

[Shenoy, 1997]

EECS 144/244, UC Berkeley: 32

## Retiming Tradeoffs

 

[Shenoy, 1997]


EECS 144/244, UC Berkeley: 33


 
## Goals of Retiming

Possible goals:


- Minimize clock period (min-period retiming)
- Minimize number of registers (min-area retiming)
- Minimize number of registers for a target clock period (constrained min-area retiming)



[Shenoy, 1997]


EECS 144/244, UC Berkeley: 34

 Abstraction:  
Circuit  $\rightarrow$  Graph




EECS 144/244, UC Berkeley: 35


## Abstraction: Registers?

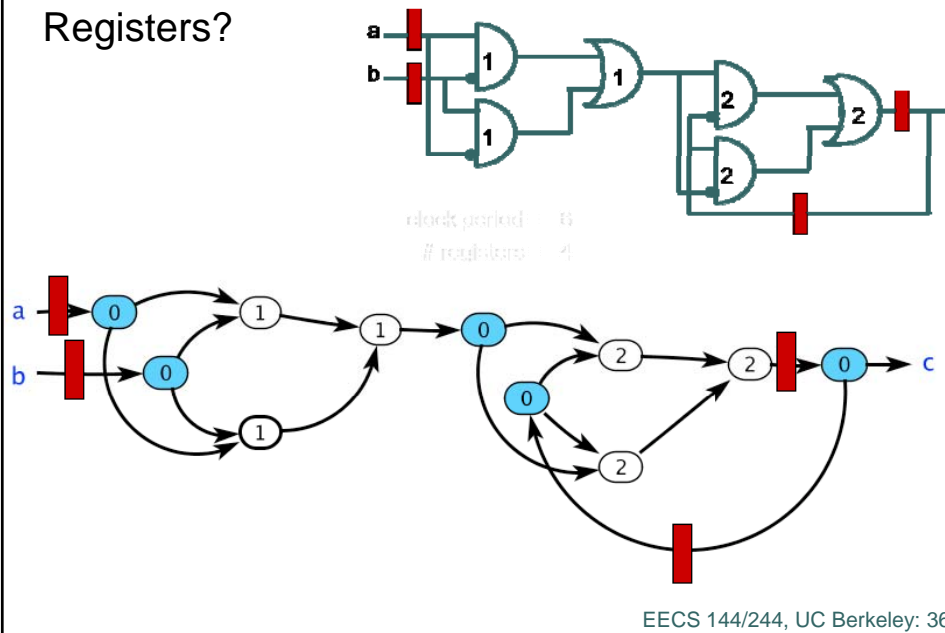

## Abstraction - Registers

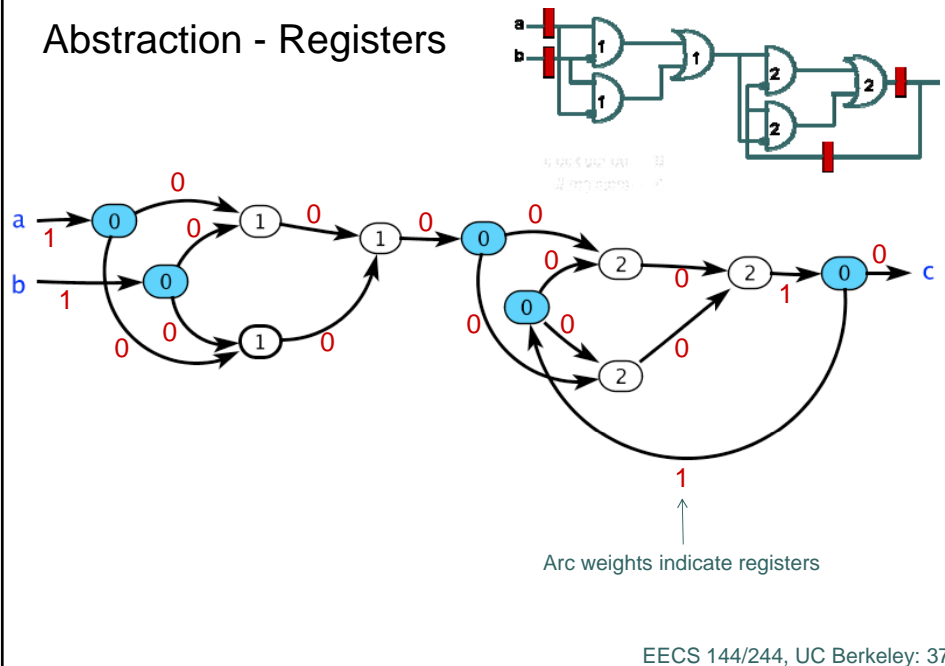


## Abstraction - Environment

 


EECS 144/244, UC Berkeley: 38

## Cutset – Divides the Graph in Two

 


EECS 144/244, UC Berkeley: 39

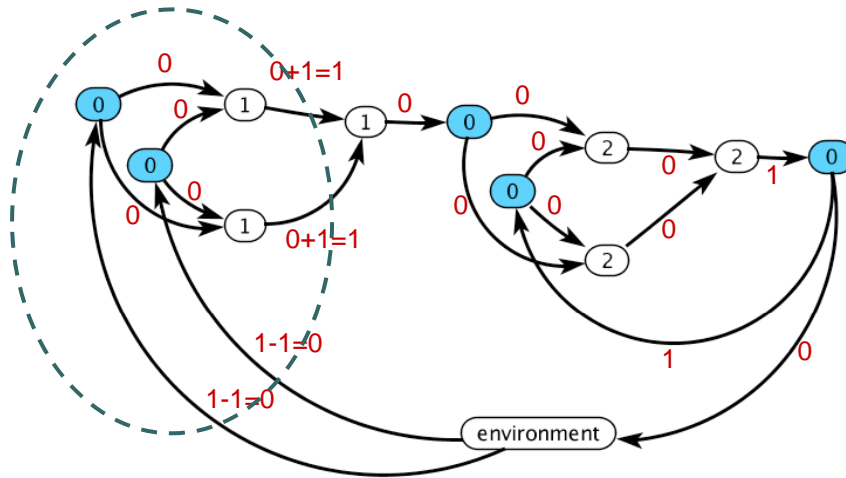Retiming: Add a register on all arcs crossing the cutset in one direction, and subtract a register from all arcs crossing the cutset in the other direction.



EECS 144/244, UC Berkeley: 40


Recall: Retiming Tradeoffs

 

[Shenoy, 1997]

EECS 144/244, UC Berkeley: 41


## Recall: Retiming Tradeoffs

 

[Shenoy, 1997]


EECS 144/244, UC Berkeley: 42

## Simplest cutset surrounds one node

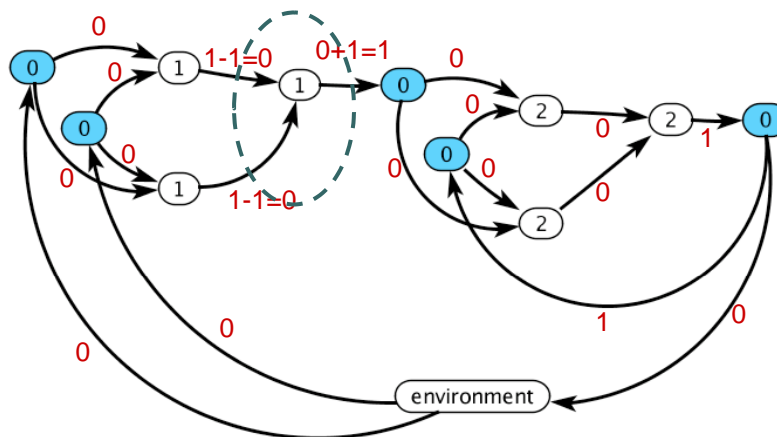

EECS 144/244, UC Berkeley: 43


## Recall: Retiming Tradeoffs

 

[Shenoy, 1997]

EECS 144/244, UC Berkeley: 44

## Recall: Retiming Tradeoffs

 


[Shenoy, 1997]

EECS 144/244, UC Berkeley: 45

For each node  $v$ , define  $r(v) = \#$  of registers moved from the outputs to the inputs.

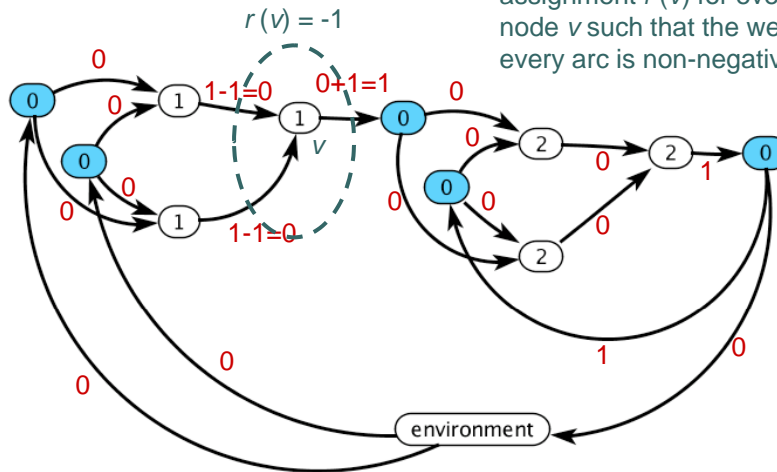A *retiming* is now an assignment  $r(v)$  for every node  $v$  such that the weight of every arc is non-negative.



EECS 144/244, UC Berkeley: 46

## Rest of the story

Retiming operations = graph transformations

Each graph has a vector of costs: (clock period, # registers, ...)

Formulate and solve optimization problem.

Papers (on bspace):

1. Leiserson, C. E. and J. B. Saxe (1983). "Optimizing synchronous systems." *Journal of VLSI and Computer Systems*: pp. 41-67.
2. Leiserson, C. E. and J. B. Saxe (1991). "Retiming synchronous circuitry." *Algorithmica* 6(1): pp. 5-35.
3. Shenoy, N. (1997). "Retiming: Theory and practice." *Integration, the VLSI Journal* 22: pp. 1-21.

EECS 144/244, UC Berkeley: 47